

$$\begin{aligned}
 1. \text{ DC gain} &= 1000 \\
 &= 20 \log 1000 \\
 &= 60 \text{ dB}
 \end{aligned}$$

$$2. \text{ GBW} = 30 \text{ MHz}$$

$$3. \text{ PM} \geq 60^\circ$$

$$4. \text{ Slew rate} = 20 \text{ V}/\mu\text{Sec}$$

$$5. \text{ ICMR}(+) = 1.2$$

$$6. \text{ ICMR}(-) = 0.5$$

$$7. C_L = 2 \text{ pF}$$

$$8. \text{ power} \leq 300 \mu\text{W}$$

$$9. V_{DD} = 1.8$$

$$10. \text{ process} = 90 \text{ nm}$$

$$L_{\min} = 90 \text{ nm}$$

$$L \geq 2 \cdot L_{\min}$$

$$L \geq 2 \cdot 90 \text{ nm}$$

$$L \geq 180 \text{ nm}$$

$$L = 500 \text{ nm}$$

$$1. L = 500 \text{ nm}$$

$$2. C_c \geq 0.22CL$$

$$C_c \geq 0.22 \times 2 \text{ pF}$$

$$C_c \geq 0.44 \text{ pF}$$

$$C_c \geq 440 \text{ fF} \quad (\text{for } PM \geq 60^\circ)$$

$$\boxed{C_c = 800 \text{ fF}} \quad (\text{for Design purpose})$$

$$3. \text{ Slew rate} = \frac{I_5}{C_c}$$

$$I_5 = S_R \cdot C_c$$

$$I_5 = 20 \text{ V}/\mu\text{sec} \times 800 \text{ fF}$$

$$I_5 = 16 \mu\text{A}$$

$$\boxed{I_5 = 20 \mu\text{A}}$$

Design of M_1 & M_2

$$g_{m1} = GBW \times C_c \times 2\pi$$

$$= 30 \text{ MHz} \times 800 \text{ fF} \times 2\pi$$

$$= 150.79 \mu$$

$$\boxed{g_{m1} = 160 \mu}$$

$$I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) \cdot (V_{GS} - V_t)^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) \cdot 2(V_{GS} - V_t)$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L} \right) \cdot (V_{GS} - V_t)$$

Squaring on both side

$$g_m^2 = \left[\mu_n C_{ox} \left(\frac{W}{L} \right) \right]^2 \cdot (V_{GS} - V_t)^2$$

$$g_m^2 = \underbrace{\left[\mu_n C_{ox} \left(\frac{W}{L} \right) \right]^2 \cdot \frac{(V_{GS} - V_t)^2}{2}}_{I_D} \times 2$$

$$g_m^2 = 2 I_D \mu_n C_{ox} \left(\frac{W}{L} \right)$$

$$\left(\frac{W}{L} \right) = \frac{g_m^2}{\mu_n C_{ox} 2 I_D} \quad (\because 2 I_D = P_D)$$


$$\left(\frac{W}{L} \right)_{1,2} = \frac{g_{m1}^2}{\mu_n C_{ox} \cdot P_D}$$


$$= \frac{1.60^2}{330 \mu \times 20}$$

$$= 3.878$$

$$\left(\frac{W}{L} \right)_{1,2} = 4$$

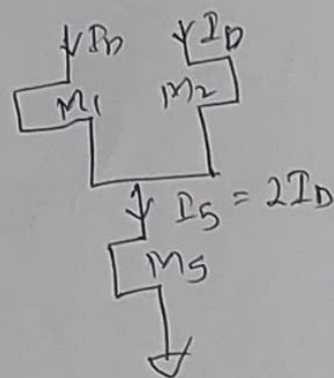Tunnig
 $\left(\frac{W}{L} \right)_{1,2} = 7$



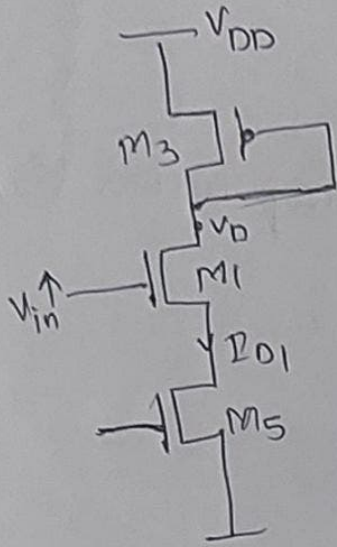Design of M_3, M_4 

\Rightarrow For a MOSFET to use as an amplifier, All the devices are/should be in Saturation region

\Rightarrow Since, M_3 is diode connected region, So M_3 , always will be in saturation region

\Rightarrow If we increase $V_{in} \uparrow$, M_1 enters into triode / linear region

\Rightarrow For, M_1 to be in saturation, then V_d of M_1 should be greater than $v_g - V_{t1}$
(gate voltage - Threshold voltage) (of M_1)
 $\therefore V_d > v_g - V_{t1}$

$$\therefore V_d > v_g - V_{t1}$$

$$V_g < V_{D1} + V_{t1}$$

$$V_{in} < V_{D1} + V_{t1} \quad (\because v_g = V_{in}) \rightarrow (\text{gate voltage} = V_{in})$$

$$V_{in} \leq V_{D1} + V_{t1}$$

For, $V_{in(max)} = V_{D1} + V_{t1}$ ——— (1)

$$I_{D3} = \frac{\mu_p C_{ox} \left(\frac{W}{L}\right)}{2} (V_{gs} - V_{t1})^2$$

(6)

$$= \frac{\beta}{2} (v_{gs} - |v_{t1}|)^2 \quad \left(\because \beta = \mu_p C_{ox} \left(\frac{W}{L} \right) \right)$$

$$\Rightarrow v_{gs} = \sqrt{\frac{2I_{D3}}{\beta}} + |v_{t3}|$$

$$V_{D1} = V_{DD} - V_{gs3} \quad (\because v_{gs3} = \text{voltage drop across } M_3)$$

$$V_{D1} = V_{DD} - \left[\sqrt{\frac{2I_{D3}}{\beta_1}} + |v_{t3}| \right] \quad \text{--- (2)}$$

from eqⁿ (1)

$$V_{in(max)} \leq \underbrace{V_{D1} + V_{t1}}_{\min} \quad \left(\text{minimum value of } V_{D1} \text{ \& } V_{t1} \text{ is equal to } V_{in(max)} \right)$$

$$ICMR + \leq V_{D1min} + V_{t1min} \quad (\because V_{in(max)} = ICMR +)$$

$$ICMR + \leq \left[V_{DD} - \underbrace{\left[\sqrt{\frac{2I_{D3}}{\beta}} + |v_{t3}| \right]}_{\substack{\uparrow \\ \text{from eq}^n - (2)} \atop (\min)} \right] + V_{t1(min)}$$

$$ICMR + \leq V_{DD} - \sqrt{\frac{2I_{D3}}{\beta}} - |v_{t3}|_{\max} + V_{t1min}$$

If V_{t3} is maximum then only the V_{D1} will be minimum

$$\frac{2I_{D3}}{\beta} = \left(V_{DD} - (I_{CMR_{max}} - |V_{t3}|_{max} + V_{t_{min}}) \right)^2$$

$$\frac{2I_{D3}}{\mu_{pcox} \left(\frac{W}{L} \right)_{3,4}} = \left(V_{DD} - I_{CMR_{max}} - |V_{t3}|_{max} + V_{t_{min}} \right)^2$$

$$\left(\frac{W}{L} \right)_{3,4} = \frac{2I_{D3}}{\mu_{pcox} (V_{DD} - I_{CMR_{max}} - |V_{t3}|_{max} + V_{t_{min}})^2}$$

$$V_{DD} = 1.8$$

$$I_{D3} = \frac{I_{D5}}{2} = \frac{20}{2} = 10 \mu$$

$$\mu_{pcox} = 170 \mu$$

$$I_{CMR} + = 1.2$$

$$V_{t3(max)} = 0.19 \mu$$

$$V_{t3(min)} = 0.22 \mu$$

$$V_{t1(max)} = 0.3 \mu$$

\Rightarrow For M_3 & M_4 V_{th} value can be taken by using arbitrary value - 10μ , 5μ (or) 15μ

\Rightarrow This value is used only to find the V_{th} value of M_1 & M_3

\Rightarrow These value are taken to compare the variation in V_{th} value of M_1 & M_3

For 10μ length

$$V_{cm} = 1.2$$

$$M_1 = 293.958m = 300m = 0.3\mu$$

$$M_3 = 186.518m \approx 190m = 0.19\mu$$

$$V_{cm} = 0.5$$

$$216.766m \approx 220m = 0.22\mu$$

$$186.518m$$

For 5μ length

$$M_1 = 294.185m$$

$$216.93m$$

$$M_3 = 186.281m$$

$$186.281m$$

$$\left(\frac{\omega}{L}\right)_{3,4} = \frac{2I_{D3}}{\mu_p C_{ox} (V_{DD} - |V_{th3}|_{max} - |V_{th1}|_{min})^2}$$

$$= \frac{2 \times 10}{170 (1.8 - 1.2 - 0.19 + 0.22)^2}$$

$$= 0.296$$

$$\left(\frac{\omega}{L}\right)_{3,4} \approx 1$$


6. Design of M_5

\Rightarrow when V_{in} decrease, v_{gs} almost remains constant and V_o decreases

$\Rightarrow M_5$ to be in saturation

$$V_{D5} > V_{gs} - V_{t5}$$

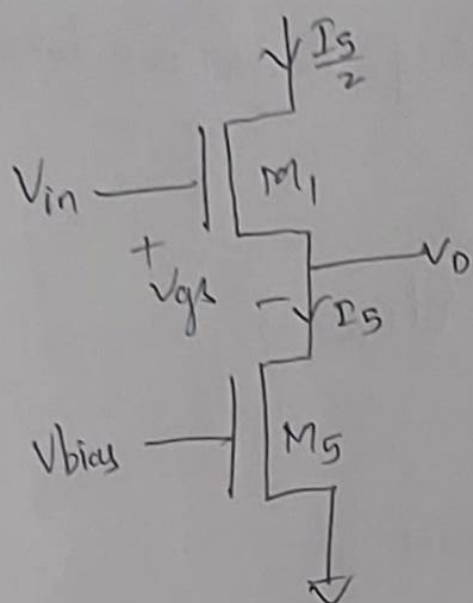\Rightarrow When V_{in} decreases, V_D of M_5 is decreasing then M_5 will enter to triode region



$\Rightarrow V_D = V_{sat} \rightarrow$ Required for M_5 to be in saturation

Therefore

$$V_{in} \geq V_{gs1} + V_{Dsat5}$$

(min)

$$ICMR - \geq V_{gs1(max)} + V_{Dsat5} \quad (\because V_{Dsat} \text{ is fixed \& } v_{gs} \text{ is max to calculate } ICMR -)$$

$$ICMR - \geq \left[\sqrt{\frac{2I_{D1}}{\beta_1}} + V_{t1} \right]_{max} + V_{Dsat5} \quad \left[\because v_{gs1} = \sqrt{\frac{2I_{D1}}{\beta_1}} + V_{t1} \right]$$

$$ICMR - \geq \sqrt{\frac{2I_{D1}}{\beta_1}} + V_{t1(max)} + V_{Dsat5}$$

(10)

⇒ Body of M_1 connected to ground but source will not be connected to ground. Therefore, threshold voltage of M_1 will vary. Hence, we take maximum threshold voltage of M_1

$$V_{Dsat} \geq I_{CMR(-)} - \sqrt{\frac{2I_{D1}}{\beta_1}} - V_{th(max)}$$

$$V_{Dsat} \geq I_{CMR(-)} - \sqrt{\frac{2I_{D1}}{\beta_1}} - V_{th(max)}$$

$$V_{Dsat} \geq 0.5 - \sqrt{\frac{2 \times 10 \mu}{330 \times 4}} - 0.3 \quad [V_{th(max)} = 0.3 \mu]$$

$$V_{Dsat} = 0.5 - 0.123 - 0.3$$

$$V_{Dsat} = 77 \text{ mV}$$


$$V_{Dsat} = 0.5 - \sqrt{\frac{2 \times 10 \mu}{330 \times 7}} - 0.3$$

$$= 0.5 - 0.0930 - 0.3$$

$$V_{Dsat} = 107 \text{ mV}$$

Tuning
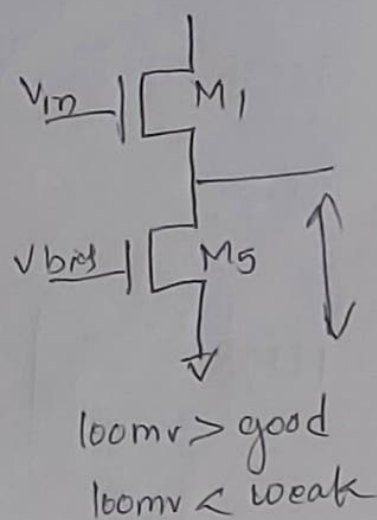
$$\left(\frac{\omega}{L}\right)_{1,2} = 7$$



$$\left(\frac{W}{L}\right)_5 = \frac{2I_{D5}}{\mu_{n\text{cox}} \cdot (V_{\text{DSAT}})^2}$$

$$= \frac{2 \times 20 \mu}{330 (107)^2}$$

$$\left(\frac{W}{L}\right)_5 = 10.58$$


$$\boxed{\left(\frac{W}{L}\right)_5 = 11}$$

Design of M_6
for 60° PM

$$g_{m6} \geq 10 \cdot g_{m1}$$

$$g_{m6} \geq 10 \cdot 160 \mu$$

$$g_{m6} \geq 1600 \mu$$

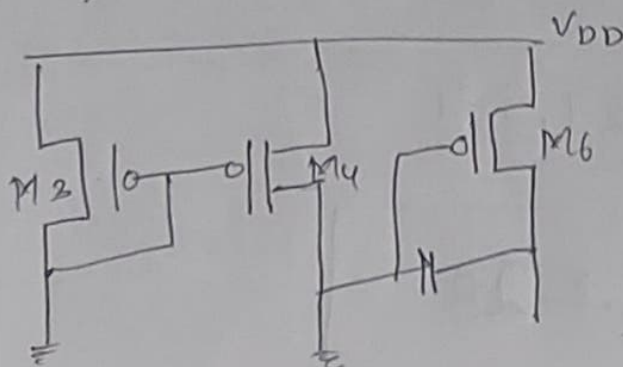

$$V_{DS} = V_{DS} = V_{DS}$$

(M3) (M4) (M6)

$$V_{GS} = V_{GS} = V_{GS}$$

(M3) (M4) (M6)

$$I_D = \mu_p C_{ox} \left(\frac{W}{L} \right) \frac{[v_{gs} - v_t]^2}{2}$$

$$\frac{\left(\frac{W}{L} \right)_6}{\left(\frac{W}{L} \right)_4} = \frac{I_6}{I_4} \quad \bigg| \quad \frac{\left(\frac{W}{L} \right)_6}{\left(\frac{W}{L} \right)_4} = \frac{g_{m6}}{g_{m4}} \quad \bigg| \quad \left(\frac{W}{L} \right)_4 = 1$$

$$g_m = \sqrt{\mu_p C_{ox} \left(\frac{W}{L} \right) \cdot 2I_D}$$

$$g_{m4} = \sqrt{170 \times 1 \times 2 \times 10}$$

$$g_{m4} = 58.30 \mu$$

$$\left(\frac{W}{L} \right)_6 = \frac{g_{m6}}{g_{m4}} \times \left(\frac{W}{L} \right)_4$$

$$= \frac{1600}{58.30} \times 1$$

$$= 27.44$$

$$\boxed{\left(\frac{W}{L} \right)_6 \approx 28}$$

Design of M_7

$$\frac{I_6}{I_4} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4}$$

$$I_6 = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} \times I_4$$

$$= \frac{28}{1} \times 10$$

$$\boxed{I_6 = 280 \mu A}$$

$$\frac{I_7}{I_5} = \frac{\left(\frac{W}{L}\right)_7}{\left(\frac{W}{L}\right)_5}$$

$$\left(\frac{W}{L}\right)_7 = \frac{I_7}{I_5} \cdot \left(\frac{W}{L}\right)_5$$

$$\left(\frac{W}{L}\right)_7 = \frac{280}{20} \times 11$$

$$\left(\frac{\omega}{L}\right)_7 = 154$$

$$\left(\frac{\omega}{L}\right)_5 = \left(\frac{\omega}{L}\right)_8$$

so. $\left(\frac{\omega}{L}\right)_5$ is 11

Therefore $\left(\frac{\omega}{L}\right)_8 = 11$

$$I_5 = 20 \mu A$$

$$C_c = 880 \text{ pF}$$

$$M_1, M_2 \Rightarrow 7 \Rightarrow \frac{3.5}{0.5}$$

$$M_3, M_4 \Rightarrow 1 \Rightarrow \frac{0.5}{0.5}$$

$$M_5 \Rightarrow 11 \Rightarrow \frac{5.5}{0.5}$$

$$M_6 \Rightarrow 28 \Rightarrow \frac{14}{0.5}$$

$$M_7 \Rightarrow 154 \Rightarrow \frac{77}{0.5}$$

$$M_8 \Rightarrow 11 \Rightarrow \frac{5.5}{0.5}$$

$$I_6, I_7 = 280 \mu A$$

Effect of current (I_{DC}):

If we increase the current then slew rate \uparrow but the gain \downarrow

because $\frac{g_m}{\lambda I_D}$ If I_D is high gain will be \downarrow

First stage gain contributed by M_1 & M_2

If we increase M_1 gain will \uparrow because $M_1 \propto g_m$ (GBW product also \uparrow)

\Rightarrow To get higher gain & GBW product increase M_1 & M_2

If we need max DCMR then we should make M_3 & M_4 \uparrow but that effect M_1 & M_2 cause gain \downarrow then we should have to make $M_5 \uparrow$

M_6 contribute gain of second stage
 M_7 contribute gain of second stage

C_c will not have effect on gain it has effect on GBW

If $C_c \downarrow$ GBW \uparrow

$C_c \uparrow$ GBW \downarrow

C_c also have big impact on slewsate

$C_c \uparrow$ SR \uparrow

$C_c \downarrow$ SR \downarrow

For ICMR $\Rightarrow 0.5$

$$g_{m1} = 167.844 \mu$$

$$g_{ds1} = 2.07644 \mu$$

$$g_{ds4} = 839.918 n$$
$$= 0.839918$$

$$g_{m6} = 1.25501 m$$
$$= 1255.01 \mu$$

$$g_{ds6} = 21.7001 \mu$$

$$g_{ds7} = 57.4821 \mu$$

$$\text{gain} = g_m (r_{o1} || r_{o4}) \quad \left. \begin{array}{l} \text{Standard} \\ \text{text book} \end{array} \right\}$$

$$\text{gain} = \frac{g_{m1}}{g_{ds1} + g_{ds4}}$$

$$= \frac{167.844}{2.07644 + 0.839918}$$

$$\text{gain} = 57.55$$

$$\text{gain in dB} = 20 \log (57.55)$$

$$\text{gain in dB} = 35.201$$

$$\text{gain} = \frac{g_{m6}}{g_{ds6} + g_{ds7}}$$

$$= \frac{1255.01}{21.7001 + 57.4821}$$

$$\text{gain} = 15.84$$

$$\text{gain in dB} = 20 \log (15.84)$$

$$\text{gain in dB} = 24.00$$

$$\text{Total gain} = \text{gain of first stage} + \text{gain of second stage}$$
$$= 59.201$$

For $V_{CMR} = 71.2$

$$g_{m1} = 181.626 \mu$$

$$g_{ds1} = 2.76759 \mu$$

$$g_{ds4} = 915.257 n$$

$$= 0.915257 \mu$$

$$\text{gain} = \frac{g_{m1}}{g_{ds1} + g_{ds4}}$$

$$= \frac{181.626}{2.76759 + 0.915257}$$

$$= 49.316$$

$$\text{gain in dB} = 20 \log (49.316)$$

$$= 33.859$$

~~Gain~~

$$\text{Total gain} = \text{gain of first stage} + \text{gain of second stage}$$

$$= 33.859 + 23.957$$

$$\text{Total gain} = 57.81$$

$$g_{m6} = 1.28827 m$$

$$= 1288.27 \mu$$

$$g_{ds6} = 22.4588 \mu$$

$$g_{ds7} = 59.2008 \mu$$

$$\text{gain} = \frac{g_{m6}}{g_{ds6} + g_{ds7}}$$

$$= \frac{1288.27}{22.4588 + 59.2008}$$

$$= 15.776$$

$$\text{gain in dB} = 20 \log (15.776)$$

$$= 23.959$$