

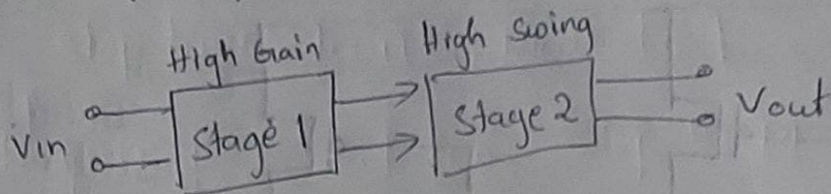


## Two stage op amp

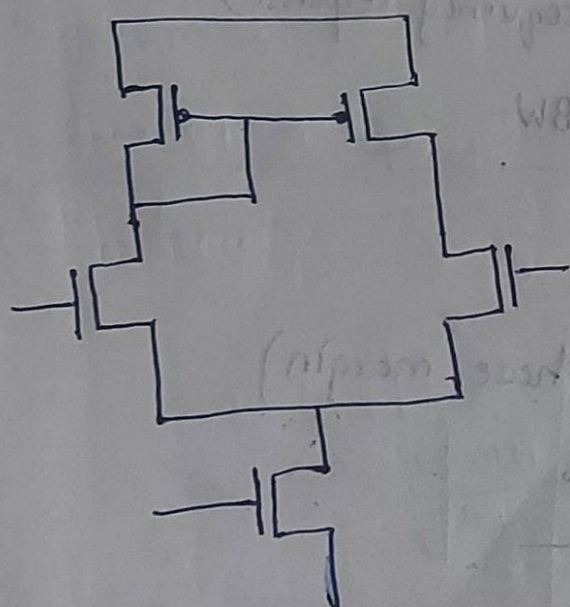


⇒ Two-stage op amp consist of first stage providing a high gain and the second providing large swing

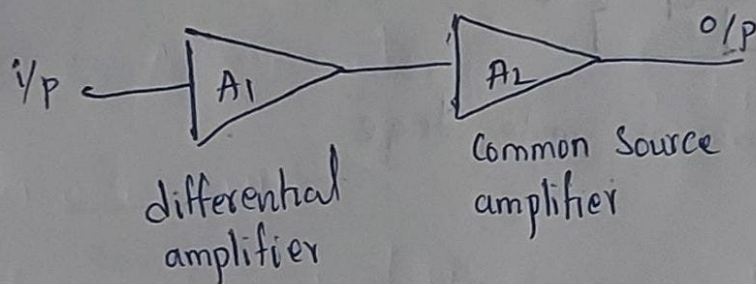⇒ The first stage incorporates various amplifier topologies, but the second stage is typically configured as a simple common source stage to allow maximum output swings. (maximum output swings ⇒ maximum output voltage)




differential amplifier

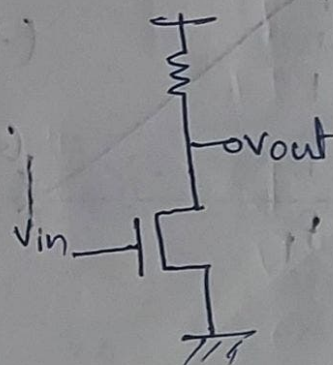

C.S n-mos amplifier

⇒ Swing is limited

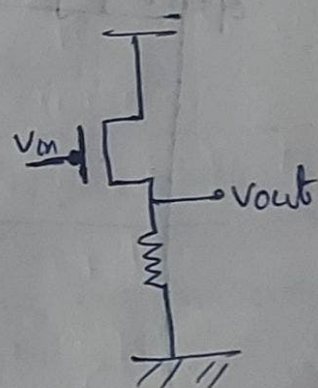

C.S P-mos amplifier

⇒ Swing is good

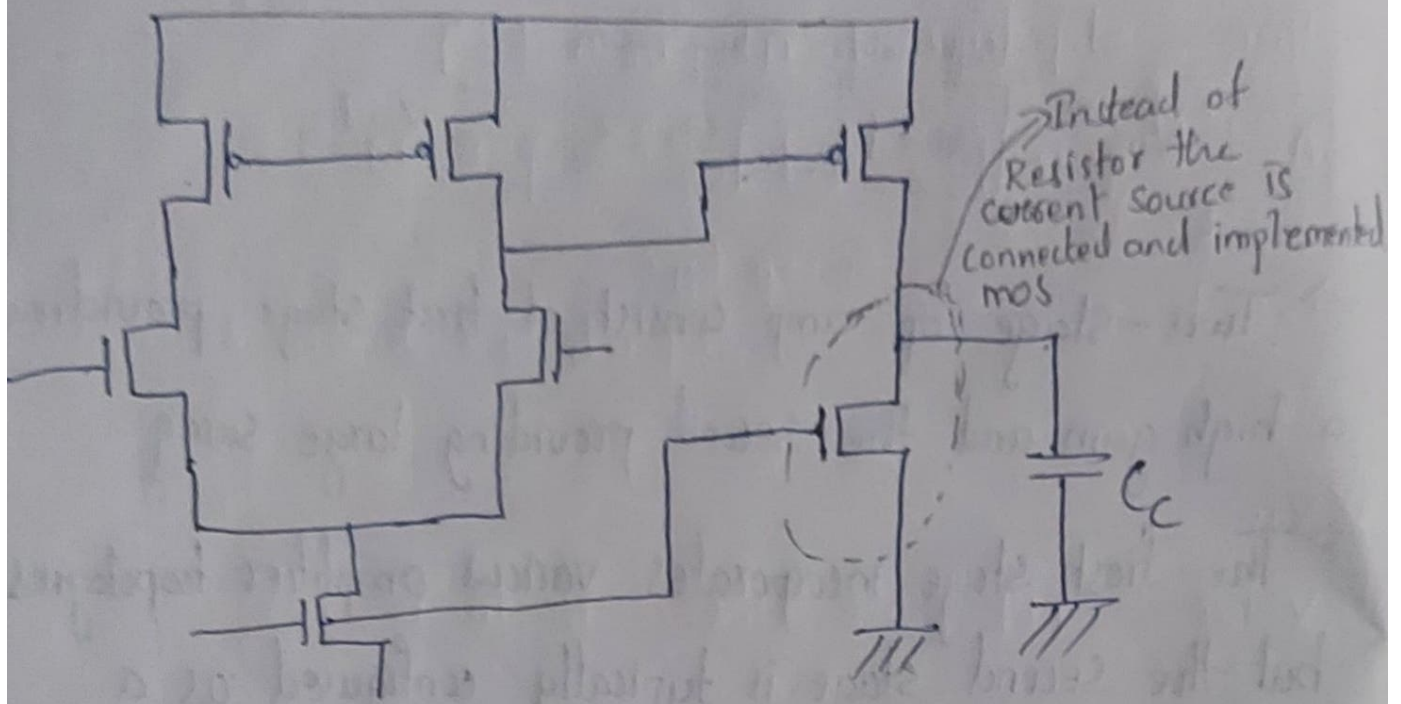


fig: Two-stage op amp

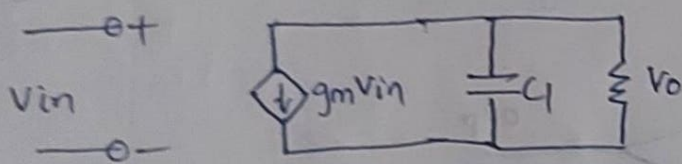


fig: Small Signal diagram of single stage

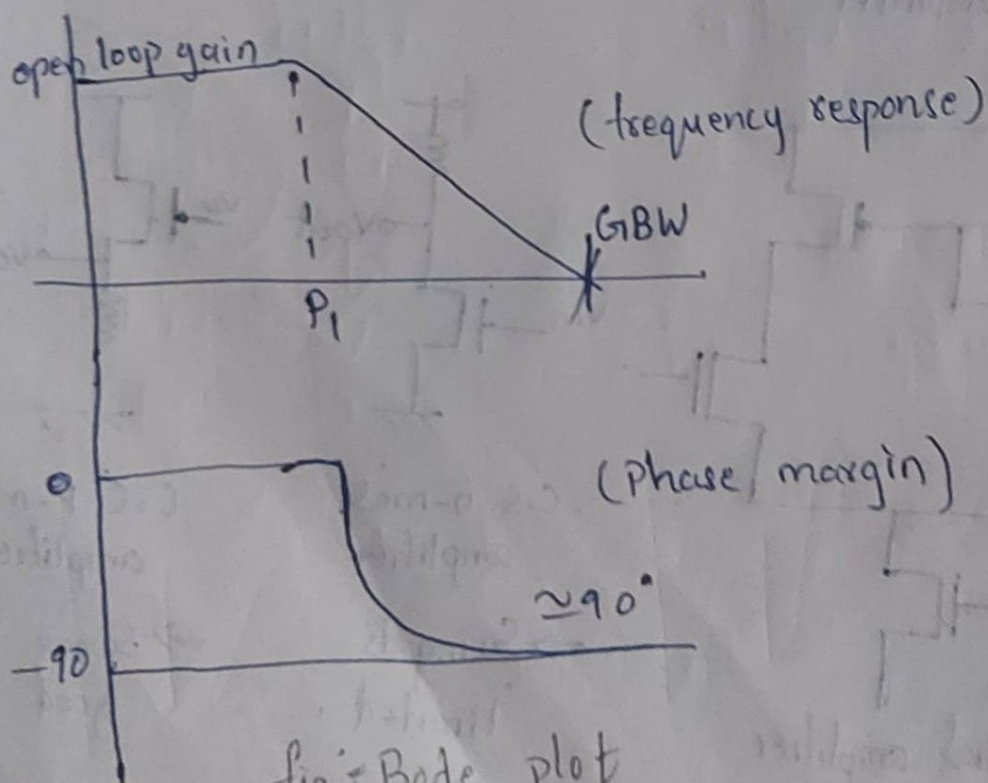


fig: Bode plot



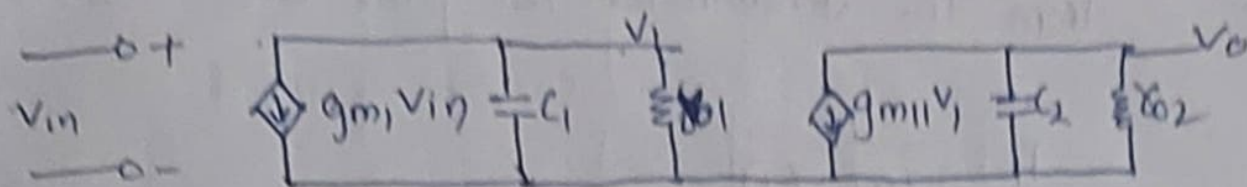


fig: Small signal diagram of two stage op amp

$$P_1 = \frac{1}{r_{o1} C_1}$$

$$P_2 = \frac{1}{r_{o2} C_2}$$

First stage output ( $V_1$ ):

At node  $V_1$ , impedance is

$$Z_1 = \left( \frac{1}{r_{o1}} \right) \parallel \left( \frac{1}{j\omega C_1} \right)$$

$$= \frac{1}{r_{o1} + j\omega C_1}$$

So,

$$V_1 = g_{m1} \cdot V_{in} \cdot Z_1$$

$$V_1 = g_{m1} \cdot V_{in} / (r_{o1} + j\omega C_1)$$

Second stage output ( $V_o$ ):

At node  $V_o$ :

$$Z_2 = \left( \frac{1}{r_{o2}} \right) \parallel \left( \frac{1}{j\omega C_2} \right)$$

$$= \frac{1}{r_{o2} + j\omega C_2}$$

So,

$$V_o = g_{m2} \cdot V_1 \cdot Z_2$$

$$V_o = g_{m2} \cdot V_1 / (r_{o2} + j\omega C_2)$$

$g_{m1}, g_{m2}$  are transconductances of stages

Sub  $V_1$  in  $V_o$

$$V_o = g_{m2} \left[ \frac{g_{m1} \cdot V_{in}}{(r_{o1} + j\omega C_1)} \right] \cdot \left[ \frac{1}{r_{o2} + j\omega C_2} \right]$$

So the overall transfer function

$$\frac{V_o}{V_{in}} = \frac{(g_{m1} \cdot g_{m2})}{(r_{o1} + j\omega C_1)(r_{o2} + j\omega C_2)}$$

from the denominator the poles are

$$P_1 = \frac{1}{(s_{o1} \cdot C_1)}$$

$$P_2 = \frac{1}{(s_{o2} C_2)}$$

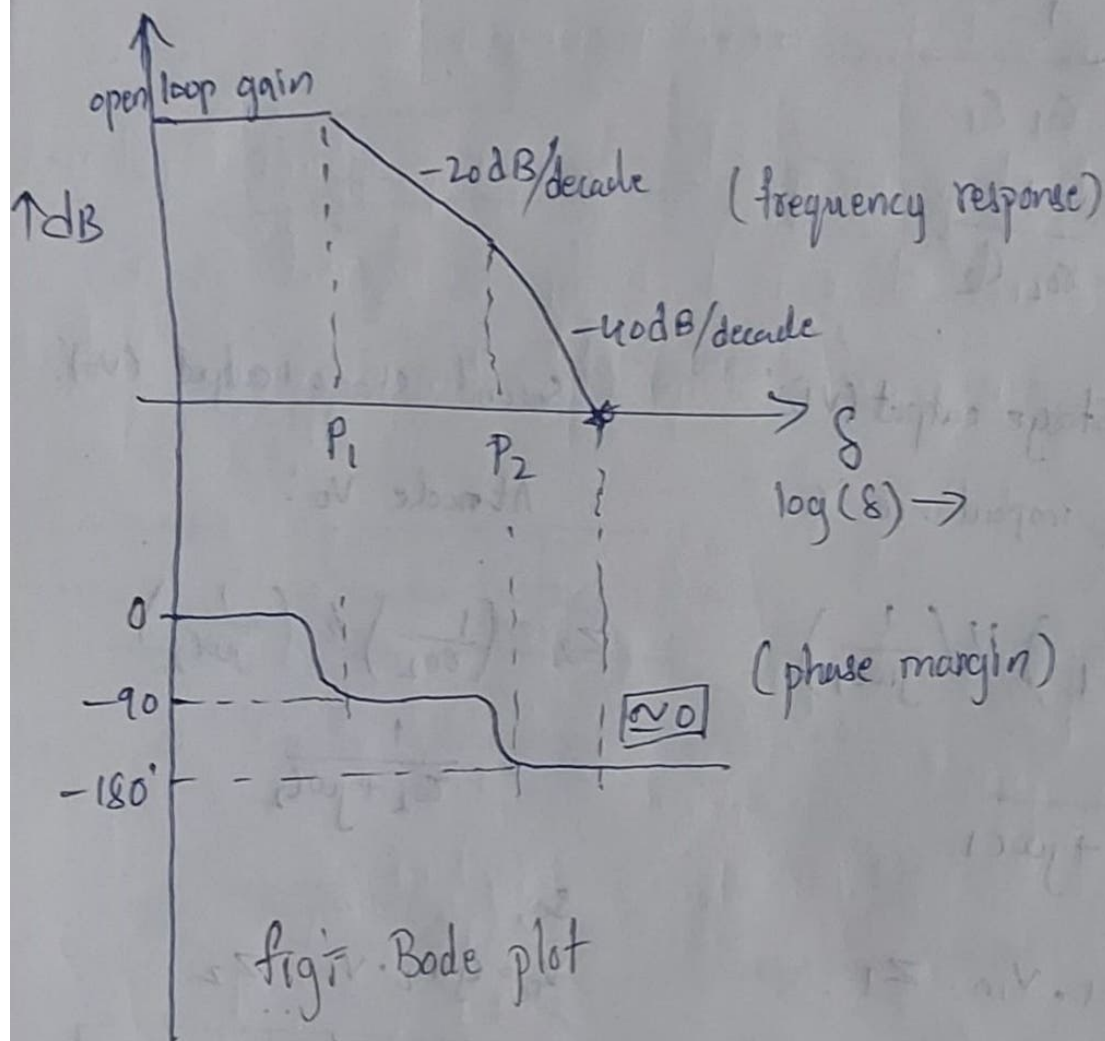


fig: Bode plot

⇒ minimum phase margin required is 45°

⇒ If it is 60° or more it is very good

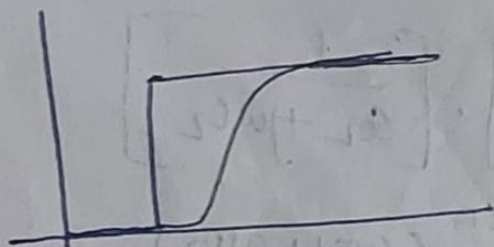


fig: for very good phase margin


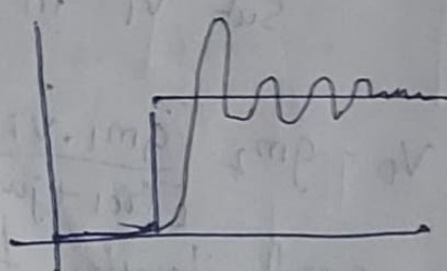


fig: for not good phase margin

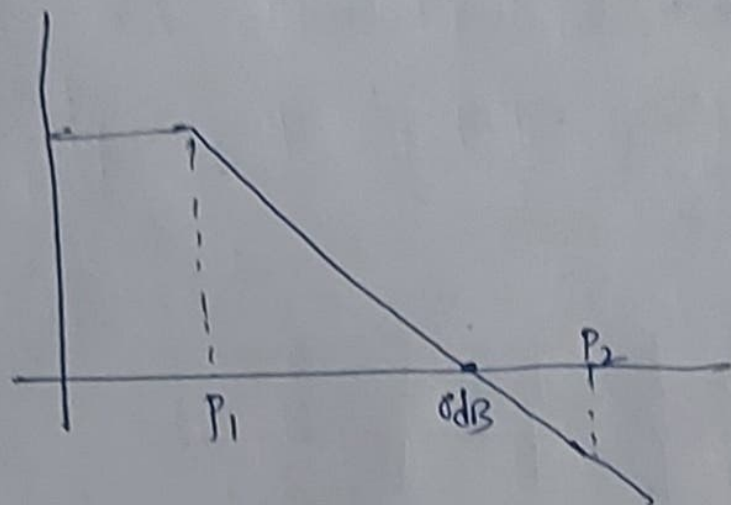⇒ Here  $P_1$  considered as dominant pole in this the Pole  $P_1$  move backward



gain excess o dB before the  $P_2$  comes

⇒ Something that comes after o dB will not have any effect so ignore that thing

⇒  $P_1$  is the dominant pole

⇒ This processes is called compensation


In  $P_1 = \frac{1}{s_{01} C_1}$  if we increase the value of  $C_1$  then we can move the Pole  $P_1$  towards left

$$\begin{aligned} \text{The } P_1 \text{ becomes } P_1 &= \frac{1}{s_{01} C_1} \\ &= \frac{1}{s_{01} (C_1 + C)} \end{aligned}$$




↗ big value

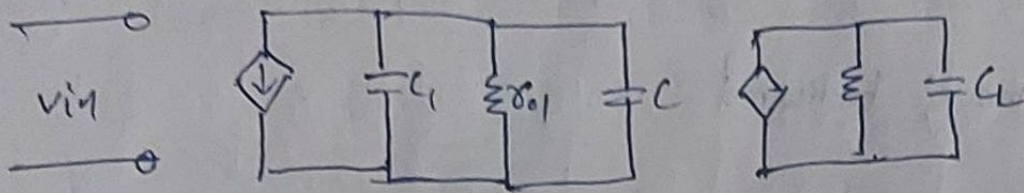⇒ here the  $C$  is what we added the value to move pole towards left.






Miller effect

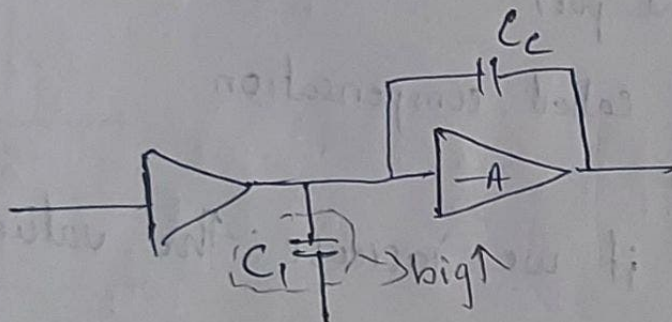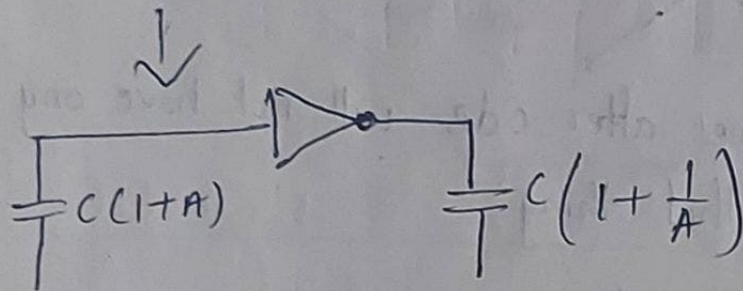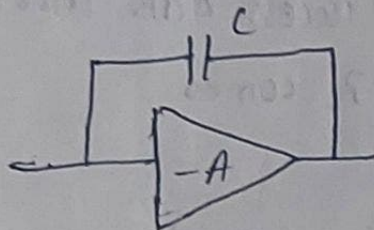

We use miller effect to get higher capacitance


Value

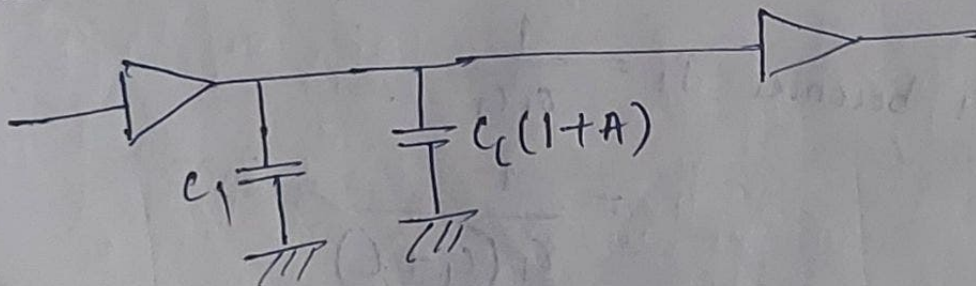

$$P_1 = \frac{1}{s_1 [C_1 + C_2(1+A)]}$$

⇒ After the miller effect is introduced the  $C_1$  value will be high this results the  $P_1$  to move towards left this is known as compensation

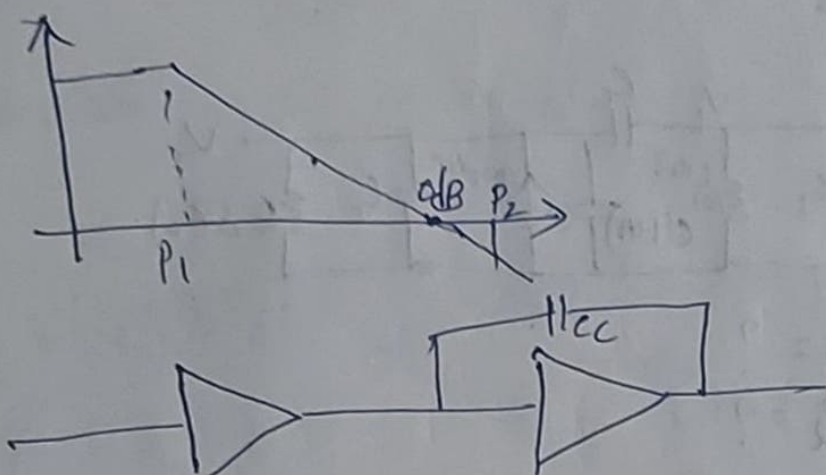⇒ The  $P_2$  will be after odb avoid the  $P_2$



$$P_1 = \frac{1}{s_{o1} [C_1 + C_c (1 + A)]}$$


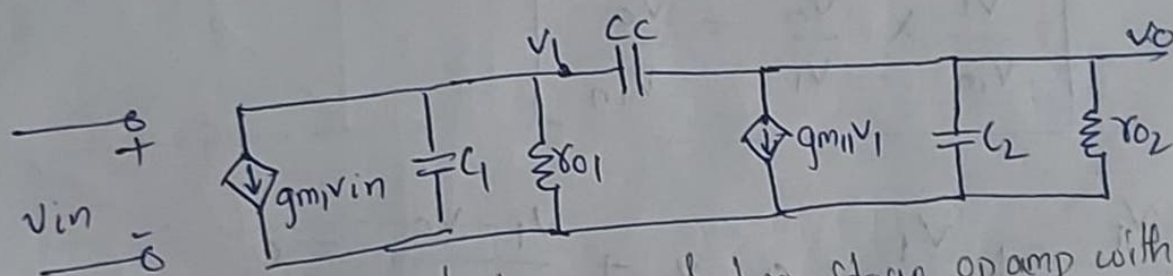


fig: Small signal diagram of two stage opamp with  $C_c$

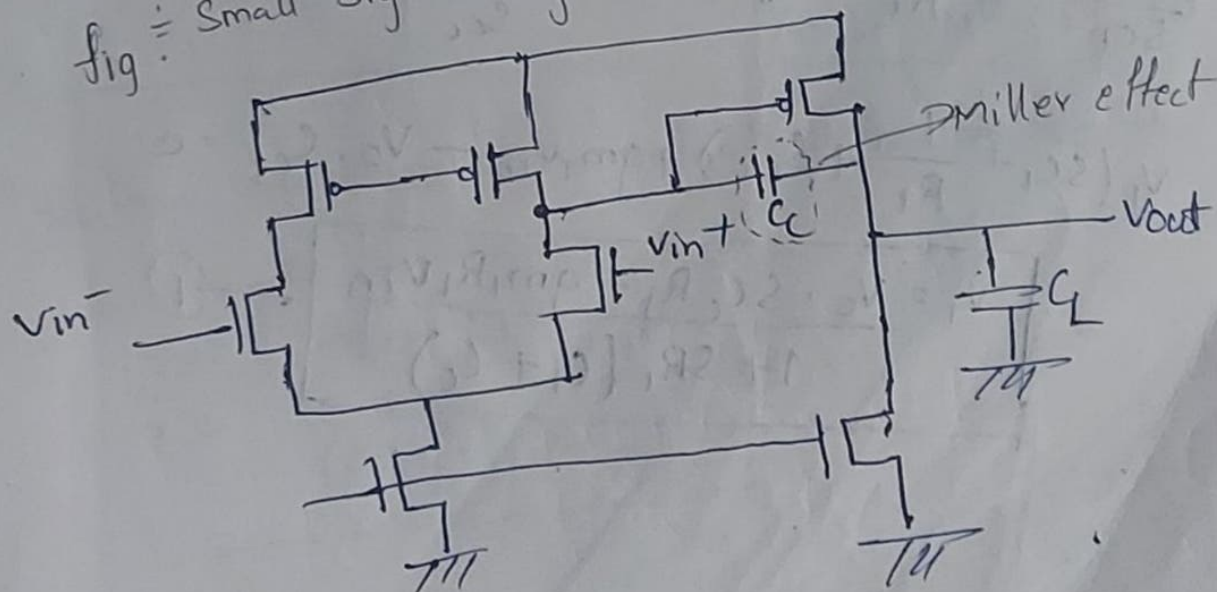




Before we go to exact design we should know the few parameters that are:

→ phase margin (Poles, zeroes, GBW etc...)

→ Slew rate

→ Swing limits

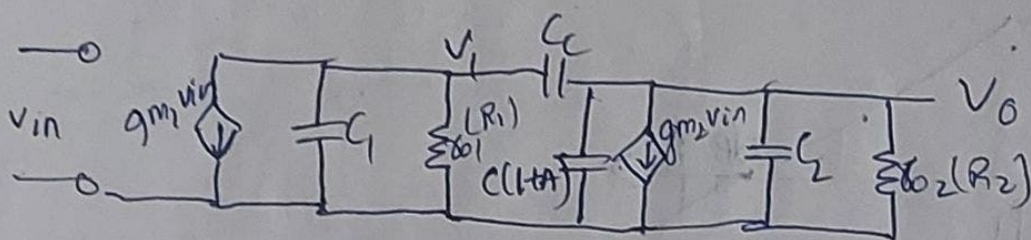

$$P_1 = ?$$

$$P_2 = ?$$

$$GBW = ?$$

$$P.m = ?$$

$$\frac{V_1}{V_{in}} \times \frac{V_o}{V_1} = \frac{V_o}{V_{in}}$$

$$\frac{V_1}{\frac{1}{sC_1}} + \frac{V_1}{R_1} + g_{m1}V_{in} + \frac{V_1 - V_o}{\frac{1}{sC_c}} = 0$$

$$V_1(sC_1 + \frac{1}{R_1} + sC_c) + g_{m1}V_{in} - V_o \cdot sC_c = 0$$

$$V_1 = \frac{V_o \cdot sC_c R_1 - g_{m1}R_1 V_{in}}{1 + sR_1(C_1 + C_c)} \quad \text{--- (1)}$$



$$\frac{V_o}{\frac{1}{sC_2}} + \frac{V_o}{R_2} + g_{m2}V_1 + \frac{V_o - V_1}{\frac{1}{sC_c}} = 0$$

$$V_o \left[ s(C_2 + C_c) + \frac{1}{R_2} \right] = V_1 (sC_c - g_{m2}) \quad \text{--- (2)}$$

Substitute eq ① in eq ②

$$V_o \left[ s(C_2 + C_c) + \frac{1}{R_2} \right] = \frac{(V_o (sC_c R_1 - g_{m1} R_1 V_{in})) (sC_c - g_{m2})}{1 + s(C_1 + C_c) R_1}$$

$$V_o \left[ s(C_2 + C_c) R_2 + 1 \right] \left[ 1 + s(C_1 + C_c) R_1 \right] = (V_o \cdot sC_c R_1 - g_{m1} R_1 V_{in}) (sC_c - g_{m2})$$

$$\boxed{\frac{V_o}{V_{in}} = \frac{g_{m1} R_1 g_{m2} R_2 \left( 1 - \frac{sC_c}{g_{m2}} \right)}{s^2 [R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c) + s [R_2 (C_1 + C_2) + R_1 (C_1 + C_c) + C_c g_{m2} R_1 R_2] + 1}}$$

For two pole system the standard transfer function

$$\boxed{\frac{V_o}{V_{in}} = \frac{A_{DC} \left( 1 - \frac{s}{\omega_z} \right)}{\left( 1 + \frac{s}{p_1} \right) \left( 1 + \frac{s}{p_2} \right)}}$$

After expanding denominator it becomes


$$= \frac{A_{oc} \left( 1 - \frac{s}{2} \right)}{1 + s \left( \frac{1}{P_1} + \frac{1}{P_2} \right) + s^2 \left( \frac{1}{P_1 P_2} \right)}$$

$$s \left( \frac{1}{P_1} + \frac{1}{P_2} \right) \approx s \frac{1}{P_1}$$

coefficient of 's'  $\Rightarrow \frac{1}{P_1}$

coefficient of 's<sup>2</sup>'  $\Rightarrow \frac{1}{P_1 P_2}$

Ex:

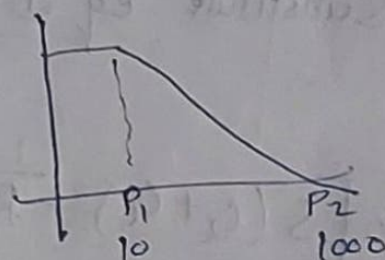

$$\frac{1}{P_1} + \frac{1}{P_2} \approx \frac{1}{P_1}$$

$$\frac{1}{10} + \frac{1}{1000}$$

$$0.1 + 0.001$$

neglect this

$$P_1 = \frac{1}{\frac{R_2(C_1 + C_2) + R_1(C_1 + C_2) + g_{m2} R_2 R_1 C_1}{\text{small} \therefore \text{neglected}}}$$

$$P_1 \approx \frac{1}{g_{m2} R_1 R_2 C_1}$$

$$P_1 P_2 = \frac{1}{R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c)}$$

$$P_2 = \frac{1}{R_1 R_2 [C_1 C_2 + C_1 C_c + C_2 C_c]} \cdot g_{m2} R_2 R_1 C_c$$

$$P_2 = \frac{g_{m2} C_c}{\underbrace{C_1 C_2 + C_1 C_c + C_2 C_c}_{\text{small} \therefore \text{neglected}}} \approx \frac{g_{m2} C_c}{C_2 C_c}$$



$$P_2 \simeq \frac{gm_2}{C_2} \quad *$$

what comes in denominator of 's' term is zero

$$Z = \frac{gm_2}{C_c} \quad *$$

$\therefore Z \Rightarrow \text{zero}$

$P_1 \Rightarrow \text{Pole 1}$

$P_2 \Rightarrow \text{Pole 2}$

In  $A_{DC}$  all the 's' are '0'

So we get

$$A_{DC} = gm_1 R_1 gm_2 R_2 \quad *$$

$$GBW = DC \text{ gain} \times P_1$$


$$= \frac{gm_1 R_1 gm_2 R_2 \times 1}{gm_2 R_1 R_2 C_c}$$

$$GBW = \frac{gm_1}{C_c} \quad *$$






$$S_R = \frac{T_o}{C_c}^*$$

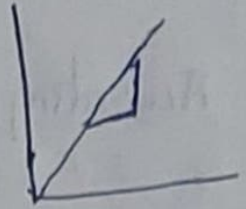

## Phase Margin

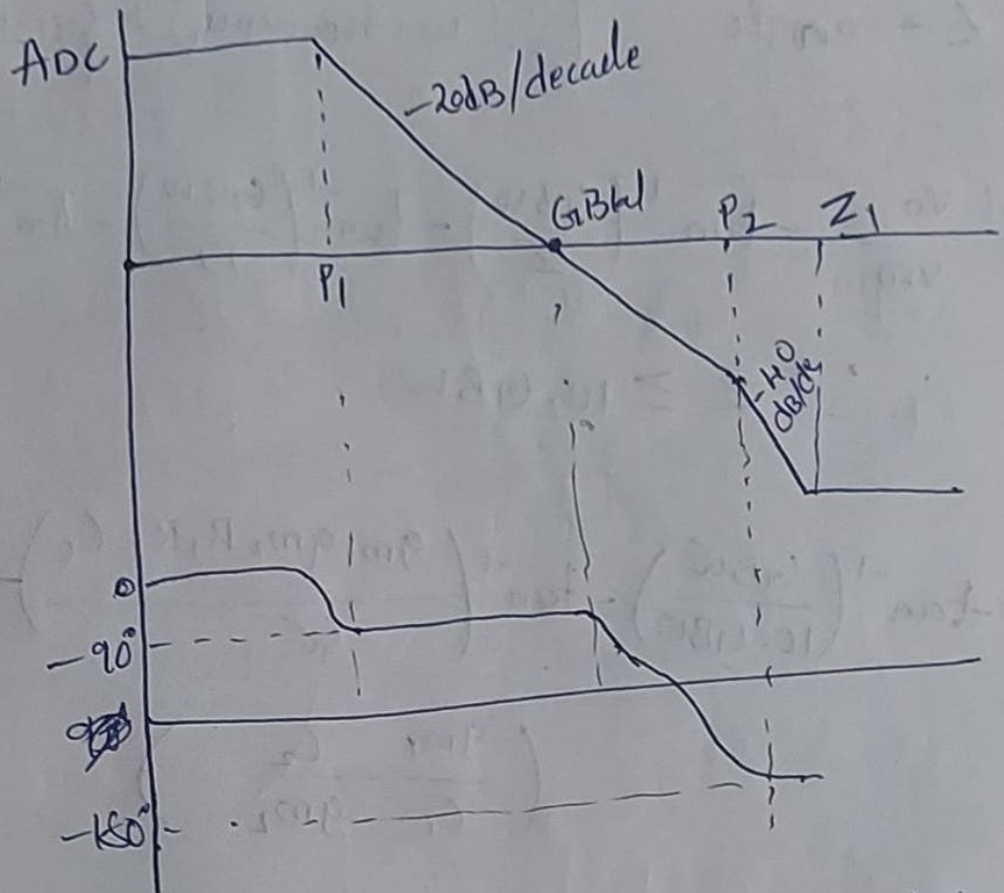

⇒ We should ensure that the phase margin should be 45° or more

⇒ To increase phase margin we move  $P_2$  towards right side

$$Z \geq 10 \cdot \text{GBW} \quad \text{--- (1)}$$

According to the standard transfer function

$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}\left(\frac{\omega}{z}\right) - \tan^{-1}\left(\frac{\omega}{P_1}\right) - \tan^{-1}\left(\frac{\omega}{P_2}\right)$$

$$\angle \rightarrow \text{angle} \quad \left[ \because \omega (\text{frequency}) = \text{GBW} \right]$$

$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}\left(\frac{\text{GBW}}{z}\right) - \tan^{-1}\left(\frac{\text{GBW}}{P_1}\right) - \tan^{-1}\left(\frac{\text{GBW}}{P_2}\right)$$

$$\therefore z \geq 10 \cdot \text{GBW}$$

$$= -\tan^{-1}\left(\frac{\text{GBW}}{10 \cdot \text{GBW}}\right) - \tan^{-1}\left(\frac{g_{m1} g_{m2} R_1 R_2 C_c}{C_c}\right) - \tan^{-1}$$

$$\left( \frac{g_{m1} C_c}{C_c g_{m2}} \right)$$

$$= -\tan^{-1}\left(\frac{1}{10}\right) - \tan^{-1}(g_{m1} g_{m2} R_1 R_2) - \tan^{-1}\left(\frac{g_{m1} C_c}{C_c g_{m2}}\right)$$

$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}\left(\frac{1}{10}\right) - \tan^{-1}(A_{DC}) - \tan^{-1}\left(\frac{\text{GBW}}{P_2}\right)$$

$$\left[ \because A_{DC} = g_{m1} g_{m2} R_1 R_2 \right]$$

$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}\left(\frac{1}{10}\right) - \tan^{-1}(A_{DC}) - \tan^{-1}\left(\frac{\text{GBW}}{P_2}\right)$$




$$-180 + PM = -5.71 - 90$$

Assume

$$-\tan^{-1}(10000) \quad [\because A_{DC} \text{ is high}]$$

$$\approx 90$$

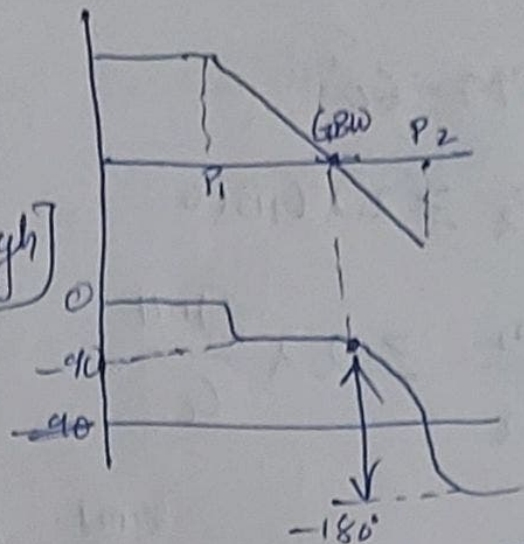

$$-180 + PM$$

$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}\left(\frac{1}{10}\right) - \tan^{-1}(A_{DC}) - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$-180 + PM = -5.71 - 90 - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$PM = 180 - 5.71 - 90 - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$PM = 84.29 - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

For  $PM = 60$

$$60 = 84.29 - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

Apply tan on b.s

$$\tan^{-1}\left(\frac{GBW}{P_2}\right) = \tan(24.29)$$

$$\frac{GBW}{P_2} = 0.4513$$

$$P_2 = \frac{GBW}{0.4513}$$

$$P_2 = 2.2 GBW$$

$$P_2 \geq 2.2 GBW$$

For  $PM = 45$

$$45 = 84.29 - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$\tan^{-1}\left(\frac{GBW}{P_2}\right) = 39.29$$

Apply tan on b.s

$$\frac{GBW}{P_2} = 0.8181$$

$$P_2 = \frac{GBW}{0.8181}$$

$$P_2 \geq 1.22 GBW$$

$$P_{10} = 60'$$

$$P_2 \geq 2.2 \text{ GBW}$$

$$\frac{g_{m2}}{C_2} \geq 2.2 \frac{g_{m1}}{C_L}$$

$$\frac{g_{m2}}{C_L} \geq 2.2 \times \frac{g_{m1}}{C_C}$$

$$\frac{10 \cdot g_{m1}}{C_L} \geq 2.2 \frac{g_{m1}}{C_C}$$

$$\frac{10}{C_L} \geq \frac{2.2}{C_C}$$

$$C_C \geq \frac{2.2}{10} C_L$$

$$\boxed{C_C \geq 0.22 C_L}^*$$

$$\left[ \because Z = \frac{g_{m2}}{C_C} \right]$$

$$\left[ \because P_2 = \frac{g_{m2}}{C_2} \right]$$

$$\left[ \because \text{GBW} = \frac{g_{m1}}{C_C} \right]$$

$$\left[ \begin{array}{l} \text{Assumed} \\ Z = 10 \cdot \text{GBW} \end{array} \right]$$

$$\frac{g_{m2}}{C_C} = \frac{10 \cdot g_{m1}}{C_C}$$

$$\boxed{g_{m2} = 10 \cdot g_{m1}}$$